

ECE 65 – Components and Circuits Lab

Lab 1 Report – Circuit Simulations

January 7, 2025

Huian Yang, Zyanya Rios

Professor: Saharnaz Baghdadchi

Table of Contents

Abstract.....	3
Experimental Procedures and Results.....	4
Problem 1: Voltage Divider (Bias Point, DC Sweep, Parametric sweep, plotting).....	4
Problem 2: RC Circuit (VPULSE function, time-domain analysis, plotting).....	14
Problem 3: Op-amp as a Voltage Amplifier (Sine function, time-domain analysis, plotting).....	23
Conclusion.....	27

Abstract

The purpose of this lab was to apply and build upon concepts learned in ECE 35 while gaining a deeper understanding of operational amplifiers (op-amps). Several experiments were conducted, including circuit analysis of a voltage divider, graphing and simulating circuits using PSpice, and exploring the behavior of inverting terminals in op-amps. The results are closely aligned with theoretical equations, enhancing our comprehension of circuit components such as op-amps and their practical applications in real-world settings.

Experimental Procedures and Results

Problem 1: Voltage Divider (Bias Point, DC Sweep, Parametric sweep, plotting)

 


Figure 1: Circuit of Voltage Amplifier

1. Calculate the Thevenin equivalent circuit of the voltage divider (the "box"). Use the Thevenin equivalent circuit to find v_o and i_o in terms of v_i , R_T and R_L . Prove that for $R_L \gg R_T$, $v_o = v_i$.

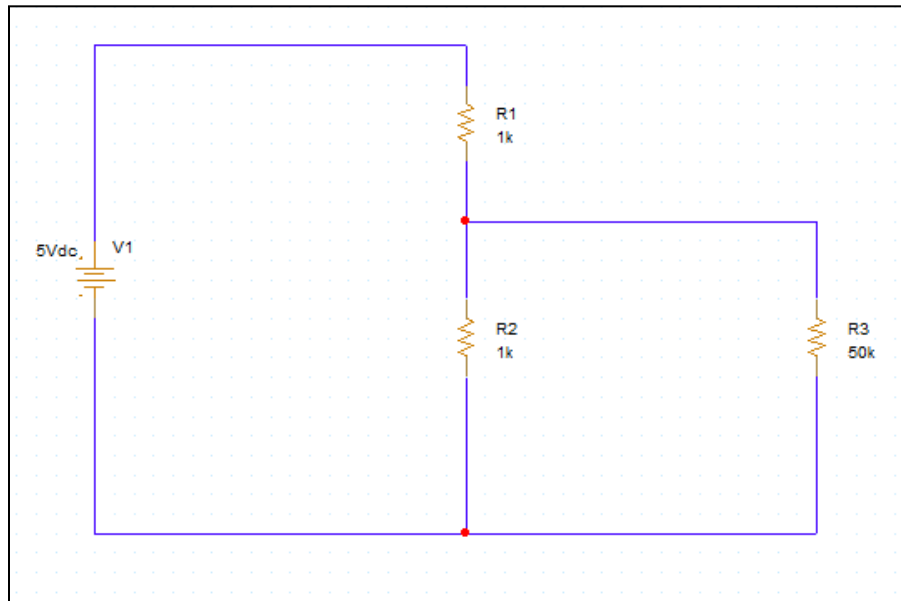


Figure 1A: Circuit Schematic of Voltage Divider Created in PSpice

In Figure 1B, we calculated the Thevenin equivalent circuit of the voltage divider (the “box”) by first calculating the Thevenin resistance. To calculate the Thevenin resistance, all the independent sources are shut off; In this circuit, there is only one DC voltage source that will be shut off. As a result, the branch that the voltage source was placed in will become shorted. Therefore that branch will have 0V. Remaining the “box” is R1 and R2 in series. Therefore Rth is equal to R1+R2.

$$R_{Th} = R_1 + R_2$$

Whereas to calculate the Thevenin voltage of the Thevenin equivalent circuit, since if we turn off all independent sources, and draw the full circuit attached with the resistor RL, it can be assumed based on a KVL, that the voltage from RL, Vo, must be equal to the Thevenin voltage circuit box because both voltages must cancel out in order for KVL to be satisfied. Therefore, by calculating Vo using a voltage divider, which is:

$$V_o = V_i \left(\frac{R_2}{R_1 + R_2} \right)$$

We can set Vth as equal to Vo, so: $V_{Th} = V_o = V_i \left(\frac{R_2}{R_1 + R_2} \right)$. V_o can also be expressed as

$V_o = R_L * i_o$ using Ohm's law.

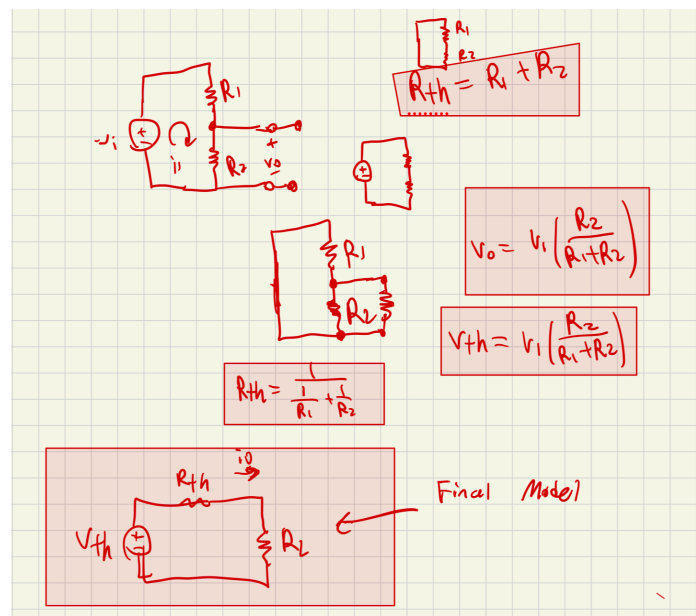


Figure 1B: Sketch of the values of Vth, Rth, and the new Thevenin Equivalent Circuit

As to why $V_o \approx V_{Th}$ when $R_L \gg R_{Th}$, figure 1C in short describes the calculations made by substituting the values of R_{Th} and i_o to show that V_o and V_{Th} arrive to the same expression of $V_i \left(\frac{R_2}{R_1 + R_2} \right)$ when $R_L \gg R_{Th}$.

Find curr. of i_o Know that $V_{Th} = V_i \left(\frac{R_2}{R_1 + R_2} \right)$

$i_o = \frac{V_{Th}}{R_{Th} + R_L}$ $R_{Th} = R_1 + R_2$

Substitute R_{Th} and V_{Th}

$R_L \gg R_{Th}$

$i_o = \frac{V_i \left(\frac{R_2}{R_1 + R_2} \right)}{(R_1 + R_2) + R_L}$ So when $R_L \gg R_{Th}$,

[Denominator simplifies to equal R_L !]

We know that $V_{Th} = V_o = i_o \cdot R_L$ Substitute in i_o

$V_o = \left(\frac{V_i \left(\frac{R_2}{R_1 + R_2} \right)}{(R_1 + R_2) + R_L} \right) R_L$ Since if $R_L \gg R_{Th}$,
[$R_1 + R_2 + R_L \approx R_L$]
Therefore the expression can be simplified to

$V_o = \frac{V_i \left(\frac{R_2}{R_1 + R_2} \right) R_L}{R_L}$

$V_o = V_i \left(\frac{R_2}{R_1 + R_2} \right)$ Which is the same expression for V_{Th} found earlier

Therefore $V_o \approx V_{Th}$ when $R_L \gg R_{Th}$

Figure 1C: Calculation as to why $V_o \approx V_{Th}$ when $R_L \gg R_{Th}$

2. Use a circuit simulator to simulate the above circuit with $R_1 = 1\text{ k}\Omega$, $R_2 = 1\text{ k}\Omega$, $R_L = 50\text{ k}\Omega$, and $v_i = 5\text{ V}$. Use "Bias Point Details" option to find the value of v_o and i_o .

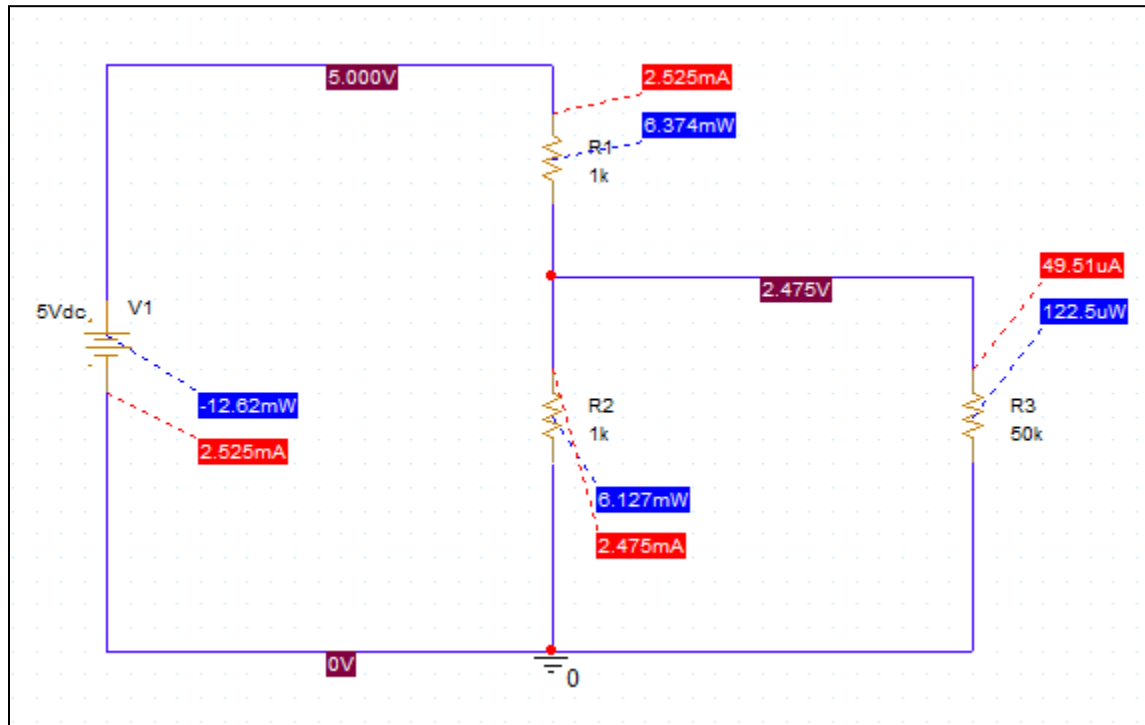


Figure 1D: Circuit Schematic of Voltage Divider Created in PSpice After Running A Bias Point Simulation

4.2 Bias Point (DC Calculations)

- 1) Analysis Type: Bias Point
- 2) Options: General Settings
 - a. For Lab #6, you will also need to select Temperature (Sweep) to run the simulation at different temperatures.
- 3) Output File Options: None
- 4) Press OK and then simulate your circuit.
- 5) To display DC bias voltages and currents on your circuit after you run the simulation, go to PSpice => Bias Points, and check Enable, Enable Bias Current Display, and/or Enable Bias Voltage Display. You should now see values on your circuit representing current and/or voltage.

Figure 1E: Set of Instructions to Create a Bias Point (DC Calculation), [Notes for ORCAD PSpice](#)

We created this circuit diagram in PSpice, using elements such as DC voltage source, resistors, ground, and wires. Once all the circuit schematic was completed, to simulate a bias point, we

referred to the UC San Diego Notes for ORCAD PSpice, and followed these steps as instructed in figure 1E.

From the circuit schematic, we observed that v_o is equal to 2.475V and that i_o is equal to 49.51 μ A.

3. Simulate the above circuit with $R1 = 1\text{ k}\Omega$, $R2 = 1\text{ k}\Omega$, and $RL = 50\text{ k}\Omega$. Use DC SWEEP to generate a plot of v_o as a function of v_i for v_i ranging from 0 to +10 V. Does it match the expression from part 1?

 


Figure 1F: Plot of V_o as a Function of V_i for V_i Ranging from 0 to 10V

4.3 DC Sweep on Input Source V_i

- 1) Analysis type: DC Sweep
- 2) Options: Primary Sweep
- 3) Sweep Variable: Voltage Source
- 4) Type in the name of the source you are sweeping.
- 5) Sweep Type: Linear (this is so you can sweep through a range of values)
- 6) Fill in the Start, End, and Increment Values. Type in 0.1V for the increment value to get a nice smooth plot.
- 7) Press OK and simulate. The simulation window should now include a place for you to plot your data. See Section 5 on how to make plots.

Figure 1G: Set of Instructions to Create a DC Sweep on Input Source V_i , [Notes for ORCAD PSpice](#)

To create this plot, we manipulated the simulation to run using the DC SWEEP to generate a plot. To set up DC SWEEP, we referred to the UC San Diego Notes for ORCAD PSpice, and followed these steps as instructed in figure 1G. Once we ran the simulation, we altered the X-axis to represent V_i ranging from 0 to +10V, and then traced V_o to generate the plot of V_o as a

function of V_i for V_o . Our results showed a linear line growing by 0.5V every following voltage increase of V_o by 1V.

This plot of V_o does match our expression from part 1 of $V_o = V_i \left(\frac{R_2}{R_1 + R_2} \right) \left(\frac{R_L}{R_L} \right)$ as it will increase and if we plug in the resistor values given and plug in V_{in} as 2V into the expression $V_o = V_i \left(\frac{R_2}{R_1 + R_2} \right) \left(\frac{R_L}{R_L} \right)$ we get that V_o is 1v, which matches with what we see on the plot.

$$V_o = (2) \left(\frac{1k\Omega}{1k\Omega + 1k\Omega} \right) \left(\frac{50k\Omega}{50k\Omega} \right) = 2 \frac{1}{2} (1) = 1V$$

4. Simulate the above circuit with $R1 = 1\text{ k}\Omega$ and $R2 = 1\text{ k}\Omega$, and $v_i = 5\text{ V}$. Use parametric SWEEP to generate a plot of v_o/v_i as a function of R_L for R_L ranging from 0 to $50\text{ k}\Omega$ (choose the increment in R_L such that you have a meaningful plot, i.e., the curve looks nice and smooth). Does it match your expectations (consider cases of $R_L \rightarrow 0$, $R_L \rightarrow \infty$, and $R_L = R_T$)?

 


Figure 1H: Plot of V_o/V_i as a function of R_L for R_L ranging from 0 to $50\text{ k}\Omega$

4.4 Parametric Sweep for Resistance

You will need to make the following changes to your circuit first:

- 1) Change the **value** of the part (not the name!) to $\{RL\}$ (use curly braces, name is arbitrary)
- 2) Go to Place => Part
- 3) Add the part PARAM/SPECIAL to your schematic
- 4) Double click on the PARAM part
- 5) Click "New Row..."
- 6) Set the name to RL (same name as in "a" but with no curly braces)
- 7) Set the value to something, e.g., 1k (this is the value that is used in calculating DC bias values, choose somewhere in the range of your sweep) and then press OK.
- 8) Select the RL column (do not double click!) so that it is highlighted and then click Display...
- 9) Select "Name and Value" and press OK.
- 10) Go back to the schematic window.
- 11) An example schematic from Lab 1 is shown below:

Figure 1I: Set of Instructions to Create a Parametric Sweep for Resistance, [Notes for ORCAD PSpice](#)

To create this plot, we manipulated the simulation to run using the Parametric SWEEP to generate a plot. To set up Parametric SWEEP, we referred to the UC San Diego Notes for ORCAD PSpice, and followed these steps as instructed in figure 1I.

The graph shown above matches with initial expectations that over time, as v_o/v_i increases and R_l increases, the voltage overall will come to a saturation point.

As R_l increases, the ratio V_o/V_i gradually rises, eventually reaching a maximum value and stabilizing at a steady-state. This behavior is consistent with the circuit's expected response as R_l approaches infinity because with a higher resistance, it's harder for current to flow through the circuit, and eventually the circuit will become an open circuit if R_l has a value of infinity.

5. Without changing the simulation settings in the previous part, plot i_o (current in R_L) versus v_o . Does it match your expectations? (consider cases of $R_L \rightarrow 0$, $R_L \rightarrow \infty$, and $R_L = R_T$)?



Figure 1J: Plot of i_o versus v_o

It did match our expectations because as R_L increases to infinity, the voltage of v_o will approach zero since an increased resistance has to be inversely proportional to current based on Ohm's law. In the case in which R_L equals 0 or near 0, the current will be near its peak since there is minimal resistance. Then in the case in which $R_L = R_T$, the current will reach a value between the minimum and maximum value of the current. These three cases help demonstrate that there is a linear relationship between i_o versus v_o .

Problem 2: RC Circuit (VPULSE function, time-domain analysis, plotting)

 


Figure 2: Circuit of RC Circuit

1. Plot v_o and v_i as a function of time for two periods for $C = 100 \text{ nF}$, $1 \text{ } \mu\text{F}$, and $10 \text{ } \mu\text{F}$.

 


Figure 2B: Circuit Schematic of RC Circuit in PSpice After Running Simulation

a. **Square Wave** is the VPLUSE function in the limit of $TR = TF = 0$ and $PW = 0.5 * PER$ (PER is the period of the wave). This limit case, however, causes numerical difficulties in calculations. In any case, we can never make such a square function in practice. In reality, square waves have very small TR and TF. Typically, we use a symmetric function, i.e., we set $TR = TF$ and $PW = 0.5 * PER - 2 * TR$. Thus, for a given frequency we can set up the square function if we choose TR. If we choose TR too large, the function does not look like a square wave. If we choose TR too small, the program will take a long time to simulate the circuit and for TR smaller than a certain value, the simulation will not converge numerically. A good choice for TR is to set it to be 1% of the PER (a period): $TR = TF = 0.01 * PER$, $PW = 0.48 * PER$. This usually results in a nice signal without a huge amount of computational need. Note that TR does not have to be exactly 1% of PER. You can choose nice round numbers for TR, TF, and PW.

Figure 2C: Set of Instructions to Set Up VPULSE function, [Notes for ORCAD PSpice](#)

To plot V_o and V_i as a function of time for two periods for different values of C , we first recreated the circuit from Figure 2 in PSpice using the elements such as wires, resistors, a capacitor, and a VPULSE voltage source.


For the settings and values of the VPULSE voltage source, we followed the instructions for setting up the square wave from the “Notes for ORCAD Spice”; First we determined that the period of the wave is equal to 0.002 because $T = \frac{1}{f}$ and the given frequency is 500 Hz, therefore $T = \frac{1}{500} = 0.002 \text{ s}$. The PW, pulse width, is equal to 0.001; This value was calculated by taking the period value times 0.48, $0.002 * 0.48 = 0.00096$. We rounded this number up to 0.001 as a result.

Then to plot the graphs, we altered the capacitance in each case or the voltage peak to peak amplitude in each case and ran a time domain analysis simulation with 2ms as our “Run To Time” option.


5V Peak to Peak Amplitude V_i

To the right, is the plot of V_o and V_i as a function of time for two periods for $C=100nF$.

 
The period of the function was determined to be 0.002 s or 2 ms because $T = \frac{1}{500 \text{ Hz}} = 0.002 \text{ s}$



1uF

 

10uF

 

2. Repeat part 1 for v_i having a peak to peak amplitude of 10 V, and zero DC bias


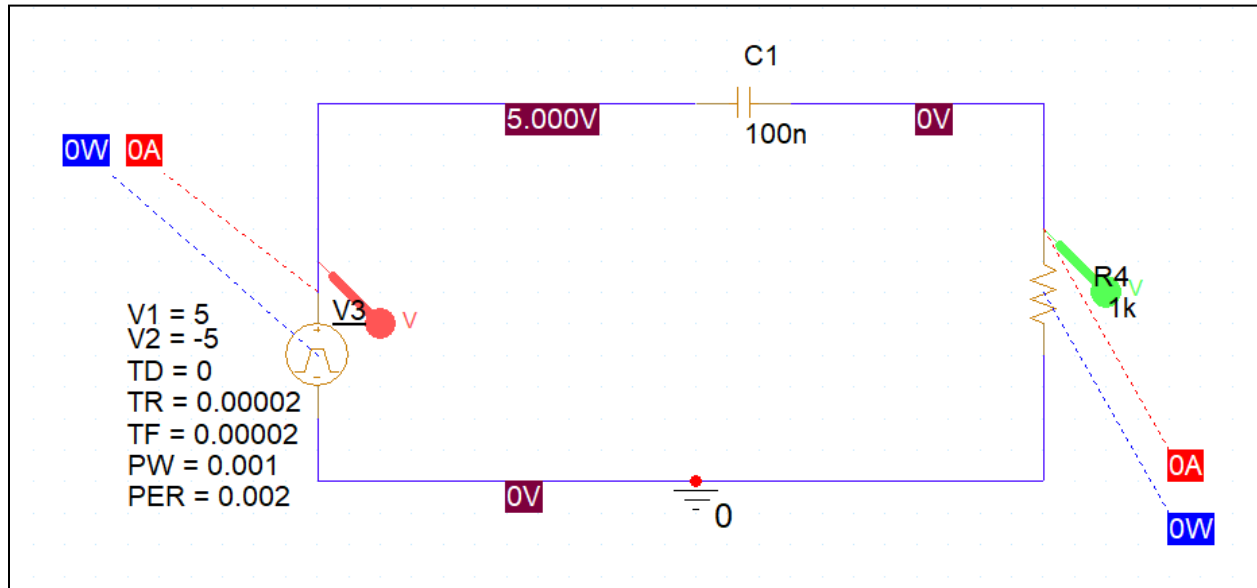


Figure 2D: Circuit Schematic of RC Circuit with a Peak to Peak Amplitude of 10V


In the figures below, the light blue represents the V_o , whereas V_i is represented by the purple square waves. For the procedure, we followed the same procedure as we did in part 2 question 1.

10V Peak to Peak Amplitude V_i


100nF

 

1uF

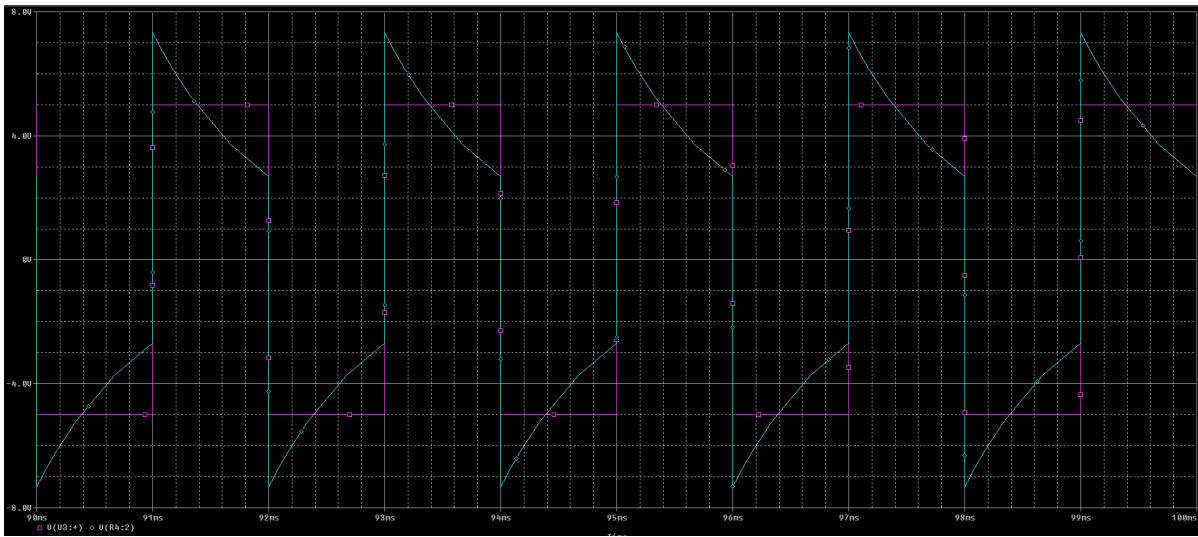

10uF

 

3. Compute the time constant, $\tau = RC$, of the three circuits (i.e., 3 different values of capacitor) and compare them to the half-period of the input voltage. What do you conclude from the above two simulations?

When $C = 100\text{nF}$, the time constant in comparison to the half-period of the input voltage is smaller than the value of the half-period of the input voltage. Given that period is equal to

$$T = \frac{1}{500} = 0.002 \text{ Hz as we calculated earlier:}$$

$$\tau = (1\text{k}\Omega)(100\text{nF}) = 0.0001 = 0.1 \text{ ms}$$

$$\text{Half-period} = \frac{T}{2} = \frac{0.002}{2} = 1 \text{ ms}$$

When $C = 1\mu\text{F}$, the time constant in comparison to the half-period of the input voltage is equal to the value of the half-period of the input voltage.

$$\tau = (1\text{k}\Omega)(1\mu\text{F}) = 0.001 = 1 \text{ ms}$$

$$\text{Half-period} = \frac{T}{2} = 1 \text{ ms}$$

When $C = 10\mu\text{F}$, the time constant in comparison to the half-period of the input voltage is roughly equal to the value of the half-period of the input voltage.

$$\tau = (1\text{k}\Omega)(10\mu\text{F}) = 0.01 = 10 \text{ ms}$$

$$\text{Half-period} = \frac{T}{2} = 1 \text{ ms}$$

From the above two simulations, we can conclude that if the time constant is smaller than the half-period (100nF case). The capacitor voltage will charge quickly to max and then discharge to

0 at a fasten rate. If the time constant is the same as the half period (1uf case). The capacitor voltage will be charged but not to max and decreased at a slow rate. Lastly, if the time constant is bigger than the half period (10uf case). Then the capacitor voltage will stay close to 0.

Problem 3: Op-amp as a Voltage Amplifier (Sine function, time-domain analysis, plotting)

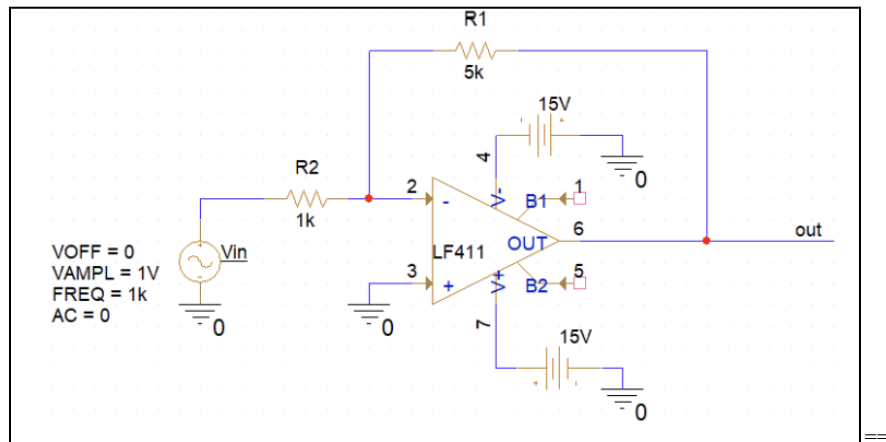


Figure 3: Circuit of Voltage Amplifier

1. Plot v_o and v_{in} as a function of time for two periods (both traces on the same plot.) Is there a linear relationship between v_o and v_i ?

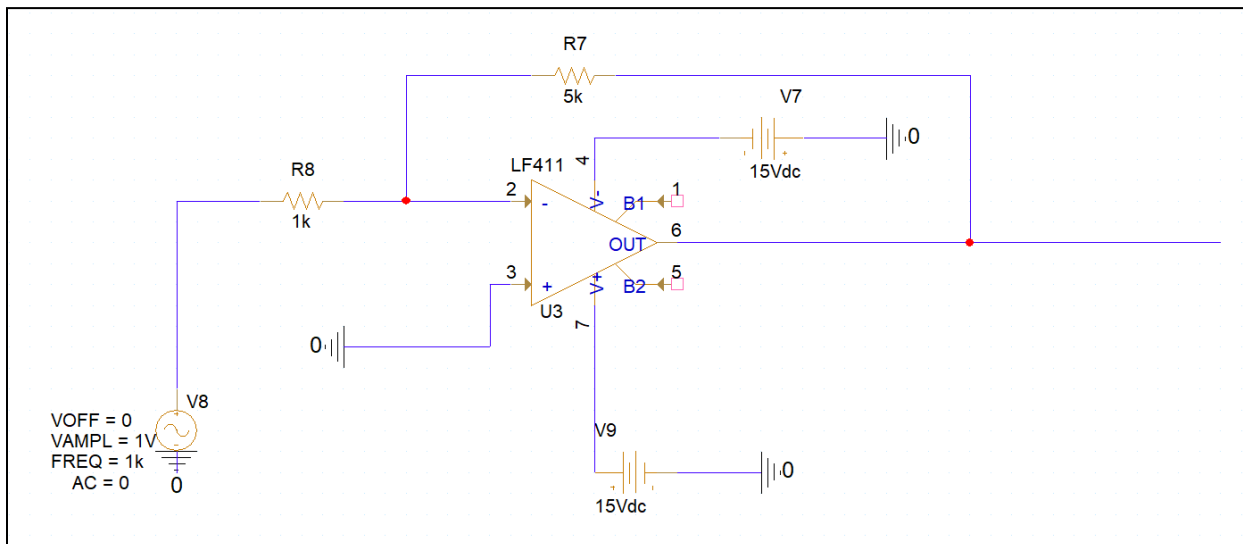


Figure 3A: Circuit Schematic of a Voltage Amplifier

 


Figure 3B: The Plot of V_o and V_{in} as a Function of Time for Two Periods

To plot V_o and V_{in} of the circuit for two periods, we first created the circuit on PSpice, using elements such as: wires, resistors, ground, DC voltage sources, an operational amplifier (LF411), and a sinusoidal input source. Once the circuit was set up, we created an environment using the time-domain feature that recorded the voltage of V_o and V_{in} for two periods. Then by using the voltage probes, we attached them to where the values of V_o and V_{in} are recorded. Our results are as shown in Figure 3B. The plot generated two sinusoidal functions

Overall we found that there is a linear relationship between V_o and V_{in} . When v_{in} is at the positive peak, v_o will be at the negative peak and vice versa. This plot reflects how a negative feedback op amp functions.

2. Plot the output current of the op-amp as a function of time for two periods.

 


Figure 3C: The Plot of the Output Current of the Op-Amp as a Function and V_{in} as a Function of Time for Two Periods

To create the plot of the output current of the op-amp as a function of time for two periods, we first calculated the time for two periods, which resulted in being 2ms. Then using a time domain analysis with a run to time from 0s to 2ms, we ran the simulation and traced the plot with the output current of the op-amp.

3. Plot of the node voltage at the input inverting terminal (V-). How does the amplitude of this node voltage compared to the amplitude of V_{in} and the node voltage at the input non-inverting terminal?

 


Figure 3D: The Plot of the Node Voltage at the Input Inverting Terminal (V-) for Two Periods

To create the plot of the output current of the op-amp as a function of time for two periods, we first calculated the time for two periods, which resulted in being 2ms. Then using a time domain analysis with a run to time from 0s to 2ms, we ran the simulation and traced the plot with the node voltage at the input inverting terminal (V-).

The amplitude of this node voltage is comparable to the voltage at the non-inverting terminal, as both are very close to 0. However, when compared to the amplitude of V_{in} , the node voltage is significantly smaller, highlighting the contrast between the two.

Conclusion

In this lab, we analyzed three distinct circuits, each with unique characteristics.

In the first experiment, we examined a voltage divider circuit with a load resistor. By determining the Thevenin voltage (V_{th}) and resistance (R_{th}), we constructed a Thevenin model and attached it to the load resistor. We concluded that when the load resistor is larger than the Thevenin resistor, the voltage drop across the load resistor significantly exceeds that across the Thevenin resistor. Using KVL, we observed that the voltage across the load resistor was closely aligned with V_{th} . Simulations in PSpice, incorporating different "sweeps," demonstrated that the voltage drop across the load resistor was linearly proportional to the load resistance. As the load resistance decreased, the voltage drop similarly decreased.

In the second experiment, we analyzed an RC circuit's response to different time constants by using three capacitors with varying capacitance values. Our observations revealed that when the time constant was less than half the period, the capacitor charged and discharged rapidly, moving from maximum voltage to zero efficiently. When the time constant was approximately equal to half the period, the capacitor struggled to reach maximum voltage and exhibited slower decay. For time constants exceeding half the period, the capacitor barely charged, resulting in small and stable voltage levels.

In the final experiment, we explored the voltage amplification capabilities of operational amplifiers. Using a sinusoidal input source and an LF411 op-amp, we constructed a negative feedback voltage amplifier. The feedback circuit fed the output back into the inverting terminal, creating an amplified yet inverted output. Simulations revealed that the node voltage at the inverting terminal (V^-) remained near zero, consistent with the grounded non-inverting terminal

(V⁺). The output voltage displayed an inverted sinusoidal waveform, showcasing the expected behavior of the op-amp.